

Northern University Of Bangladesh

Experiment No-4: Emitter bias network

Name : Fardeen Ahmed

Id : 41210301615

Semester : 5

Section : A

Course Name: Electronic Engineering Lab


Course Code: CSE 2161

Transistor:

A transistor is a type of semiconductor device that can be used to conduct and insulate electric current or voltage. There are 3 parts of a transistor.

- 1) Base : This is used to activate the transistor.
- 2) Emitter : It is the negative lead of the transistor.
- 3) Collector : It is the positive lead of the transistor.

Lets consider this circuit

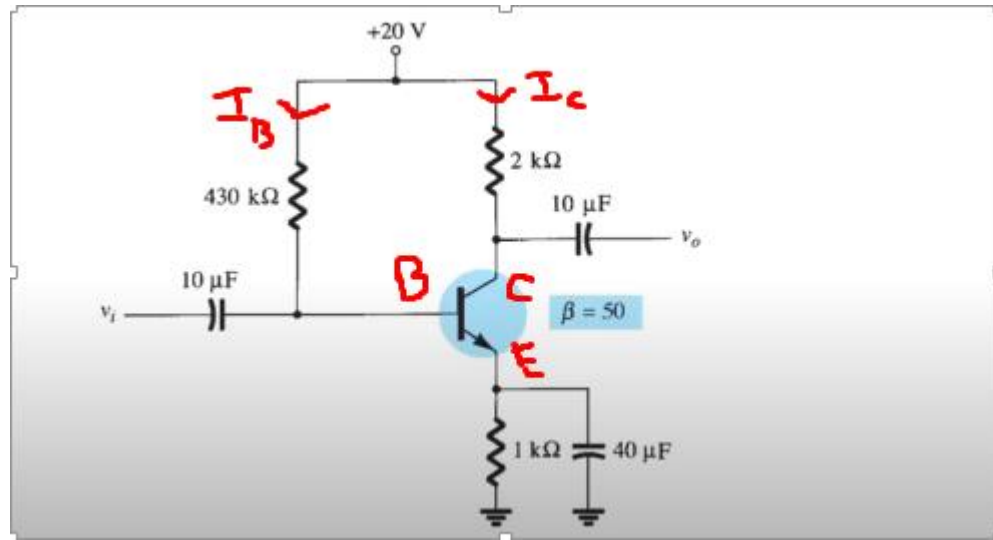

Here , $V_{CC} = 20V$
 $R_B = 430 \text{ k}\Omega$
 $R_C = 2 \text{ k}\Omega$
 $R_E = 1 \text{ k}\Omega$
 $V_{BE} = 0.7$
 $\beta = 224.5$

Now,


$$V_{CC} = I_B R_B + V_{BE} + I_E R_E \dots\dots\dots i$$

$$\begin{aligned} I_E &= I_B + I_C \\ &= I_B + \beta I_B \\ &= (1 + \beta) I_B \dots\dots\dots ii \end{aligned}$$

From i and ii

$$\begin{aligned} V_{CC} &= I_B R_B + V_{BE} + (1 + \beta) I_B R_E \\ V_{CC} - V_{BE} &= I_B (R_B + (1 + \beta) R_E) \\ I_B &= (V_{CC} - V_{BE}) / (R_B + (1 + \beta) R_E) \\ &= (20 - 0.7) / (430 \text{ k}\Omega + (1 + 224.5) 1 \text{ k}\Omega) \\ &= 29.9 \text{ }\mu\text{A} \end{aligned}$$
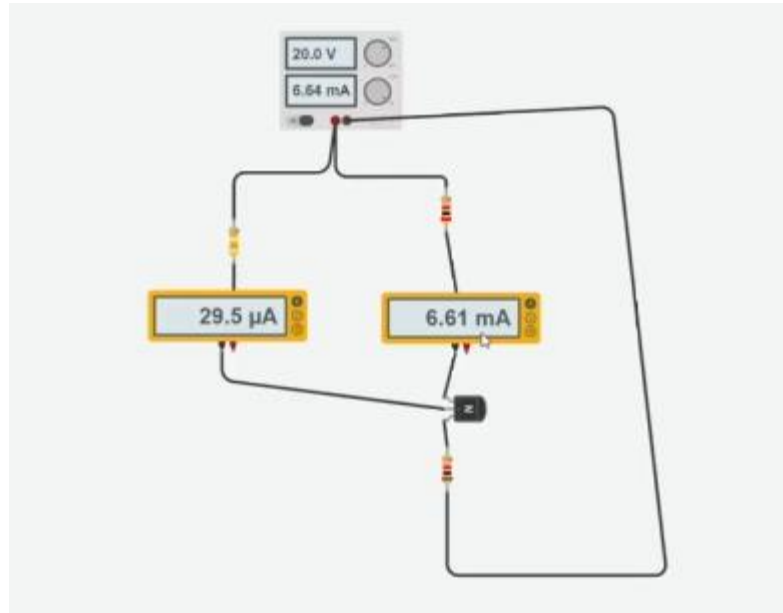
$$\begin{aligned}
 I_C &= \beta I_B \\
 &= 224.5 \times 29.9 \\
 &= 6.71 \text{ mA}
 \end{aligned}$$



Here I_B is 29.5 μA and I_C is 6.61 mA. Which is closely of 29.9 μA and I_C is 6.71 mA.

$$\begin{aligned}
 V_{CC} &= I_C R_C + V_{CE} + I_E R_E \\
 V_{CE} &= V_{CC} - I_C R_C - I_E R_E \\
 &= 20 - 6.61 \times 2 \text{ k}\Omega - 6.64 \times 1 \text{ k}\Omega \\
 &= 127 \text{ mV}
 \end{aligned}$$

