

Northern University Of Bangladesh

Experiment No-4: verification of Thevenin's theorem

Name : Fardeen ahmed

Id : 04210301615

Semester : 8

Section : A

Course Name : Electrical Engineering & Circuit Analysis Lab Course

Code : CSE 1259

Result and Discussion:

Thevenin's theorem : Thevenin's theorem states that it is possible to simplify any linear circuit, irrespective of how complex it is, to an equivalent circuit with a single voltage source and a series resistance. There are three steps to solve thevenin's theorem


- 1) Find the Thevenin Resistance by removing all voltage sources and load.
- 2) Find the Thevenin Voltage by reconnecting the voltage sources.
- 3) Use the Thevenin Resistance and Voltage to find the total current flowing through the load.

Lets consider this circuit




Lets solve this circuit using thevenin's theorem

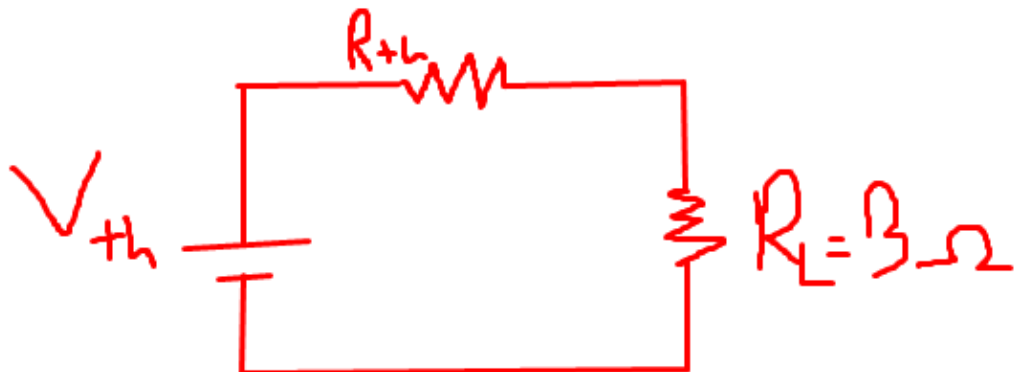At first lets draw a thevenin's equivalent circuit



Here V_{th} is thevenin's voltage , R_{th} is thevenin's resistance and R_L is load resistance .

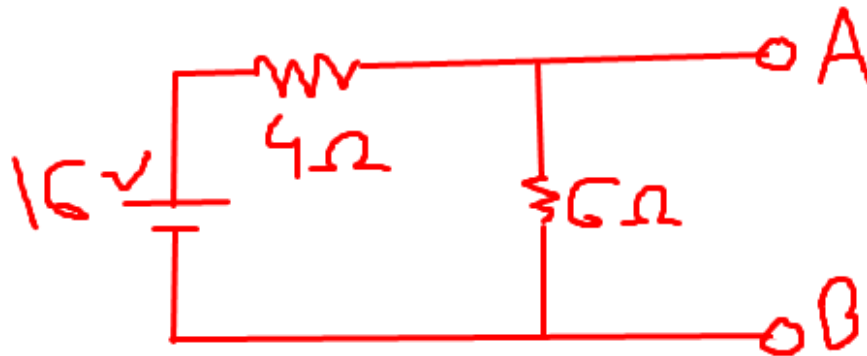According to thevenin's theorem we need to remove R_L form main circuit and calculate V_{th} and R_{th} .



Calculating V_{th} :

V_{th} will be the voltage through the resistance 6Ω


So, $I = V / R = 16 \text{ V} / (4 \Omega + 6 \Omega)$

$$= 1.6 \text{ A}$$

$$V_{6\Omega} = I \times R = 1.6 \text{ A} \times 6 \Omega = 9.6 \text{ V}$$


Calculating R_{th} :

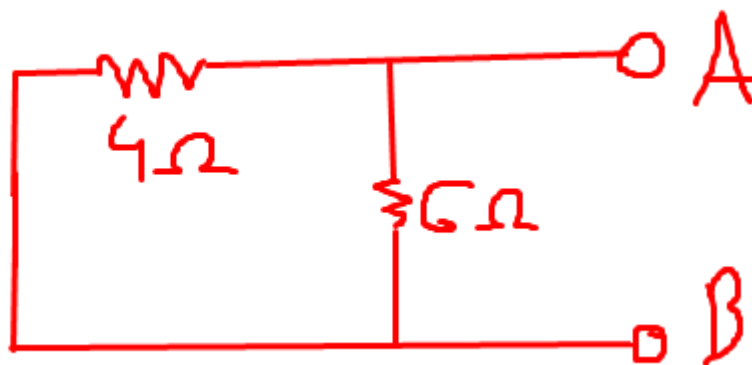To calculate according to thevenin's theorem we need to remove voltage from the circuit.



$$R_{th} = 4 \Omega \parallel 6 \Omega = 2.4 \Omega$$


So ultimately the circuit will be

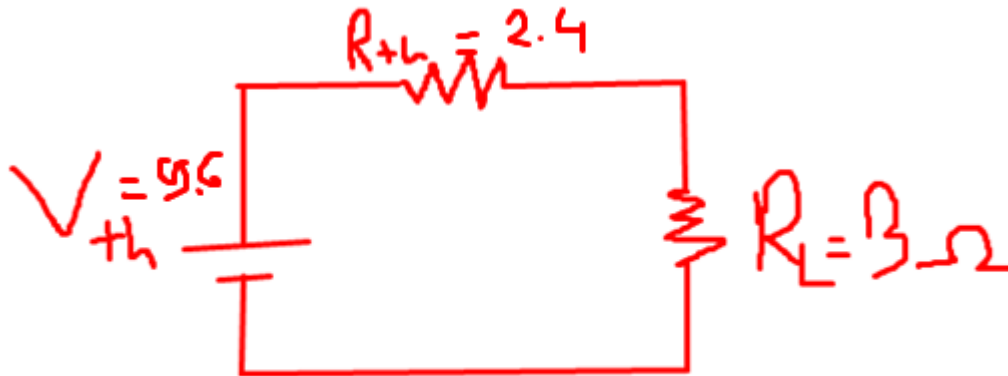

Now we need to calculate the voltage through $R_L = 3\ \Omega$ resistor

$$\text{So, } I = V / (R_{th} + R_L) = 9.6\text{ v} / (2.4\ \Omega + 3\ \Omega) \\ = 1.78\text{ A}$$
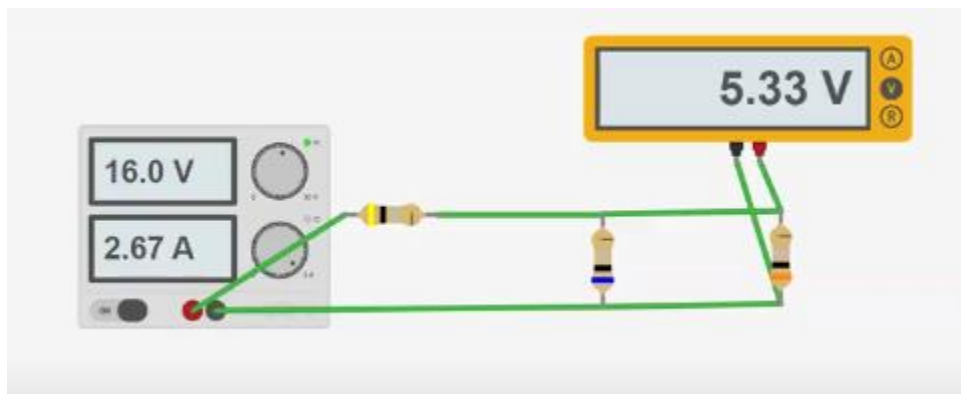
$$V_{RL} = I \times R_L = 1.78 \times 3 = 5.33\text{ V}$$



Here R_L also 5.33 V. So it can be said that thevenin's theorem is verified .