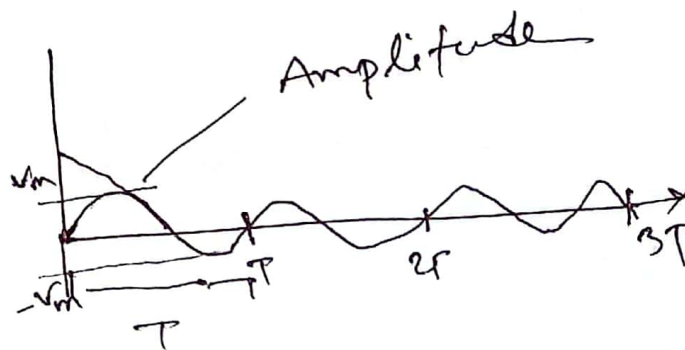


Date: 23-03-2020

AC circuit Analysis

Sinewave:



$$V_m - (-V_m) = 2V_m$$

$$\Rightarrow T = \frac{1}{f}$$

~~seconds~~ \rightarrow $V_m = \text{second}$

And $\omega = 2\pi f$

$$f = 50 \text{ Hz}$$

$$\therefore T = \frac{1}{f} = \frac{1}{50} = 0.02 \text{ s}$$

* A sinewave is a signal that has form of the sine and cosine function.

$$v(t) = V_m \sin(\omega t + \phi)$$

\downarrow Amplitude \downarrow Angular frequency
 signal

Phase

$$= 10 \sin(5t + 60^\circ)$$

for -20°

$$= \sin(\omega t + 20)$$

for $+20^\circ$

$$= \sin(\omega t - 20)$$

$$V_m = 10 \text{ V}$$


$$\phi = 60^\circ$$

$$\omega = 5 \text{ rad/s}$$

$$\Rightarrow 5 = 2\pi f$$

$$\therefore f = \frac{5}{2\pi} = 0.79 \text{ Hz}$$
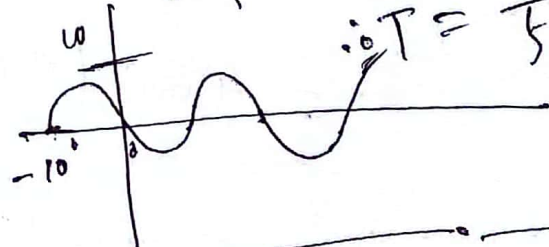
$$\therefore T = \frac{1}{f} = 1.26 \text{ s}$$



N.B

$$\sin(\omega t \pm 180^\circ) = -\sin \omega t$$

$$\cos(\omega t - 180^\circ) = -\cos \omega t$$

$$\sin(\omega t \pm 90^\circ) = \pm \cos \omega t$$

$$\cos(\omega t \pm 90^\circ) = \mp \sin \omega t$$


Apply the rule:

$$v_1 = -10 \cos(\omega t + 50^\circ)$$

$$= 10 \sin(\omega t + 50^\circ - 90^\circ)$$

$$= 10 \sin(\omega t - 40^\circ)$$

v_2 lead by v_1 by 30°

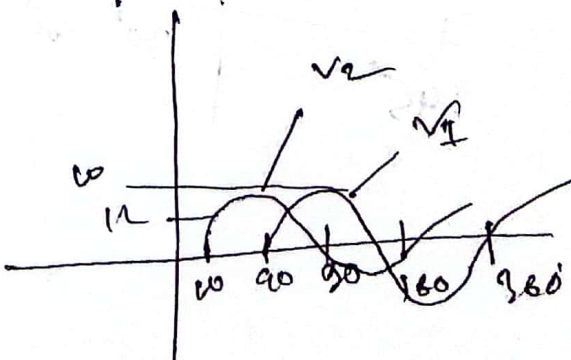

Q.2 Given that,

$$i_1 = -4 \sin(377t + 55^\circ)$$

$$i_2 = 5 \cos(377t - 65^\circ)$$


Hence, $i_1 = -4 \sin(377t + 55^\circ)$

$$= 4 \sin(377t + 55^\circ + 90^\circ)$$


$$= 4 \sin(377t + 145^\circ)$$

$$i_2 = 5 \cos(377t - 65^\circ)$$

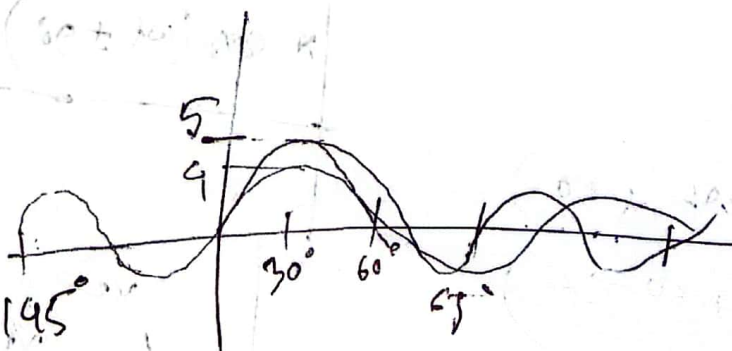$\therefore i_2$ leads for $(145 - (-65))$
 $= 210^\circ$ Ans.



Date: 25-03-24

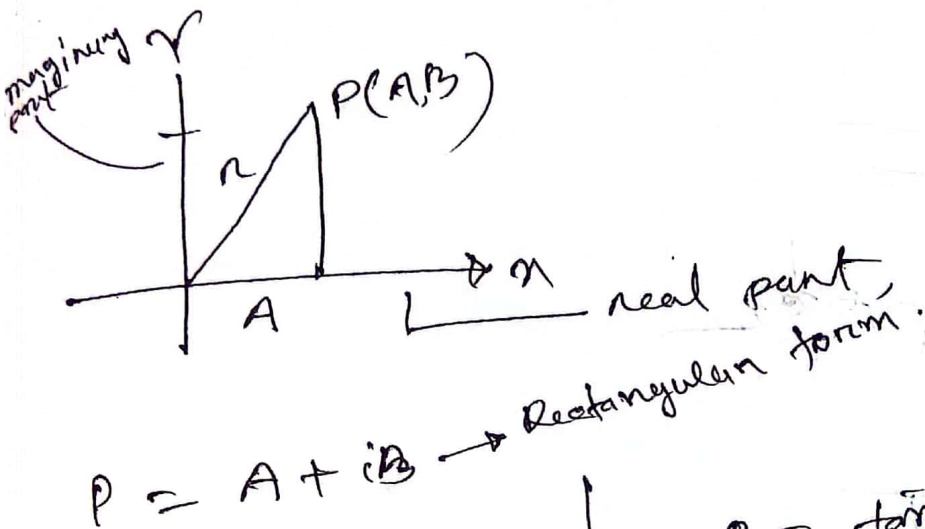

$r = \sqrt{A^2 + B^2}$ | $\phi = \tan^{-1} \frac{B}{A}$
 $P = r \angle \phi \rightarrow \text{Polar form}$
Phasor: A phasor is a complex number that represents the amplitude and phase of a sinusoid.

$$v(t) = v_m \cos(\omega t + \phi)$$


$$v(t) = v_m \angle \phi$$

Q: How to write polar form?


Date: 30-03-20

Equivalent capacitance;

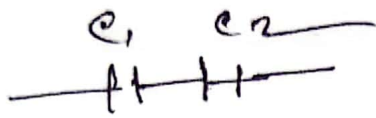inductance \rightarrow same as resistance


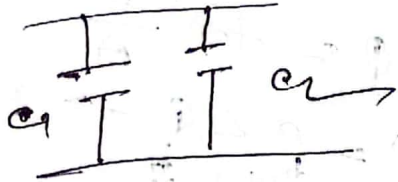
$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2}$$



$$C_{eq} = C_1 + C_2$$

impedance: $Z = R + jX$ $\rightarrow (X_L + X_C)$

$$Z = R + jX$$

Resistance
 Ω

Reactance
 Ω

\therefore total impedance Ω

capacitance Reactance:

$$X_C = \frac{1}{j\omega C}$$

$$= \frac{1}{j2\pi f C}$$

$$= \frac{1}{T} \Omega$$


Inductive Reactance:

$$X_L = j2\pi fL$$

$$= j\omega L$$



gms

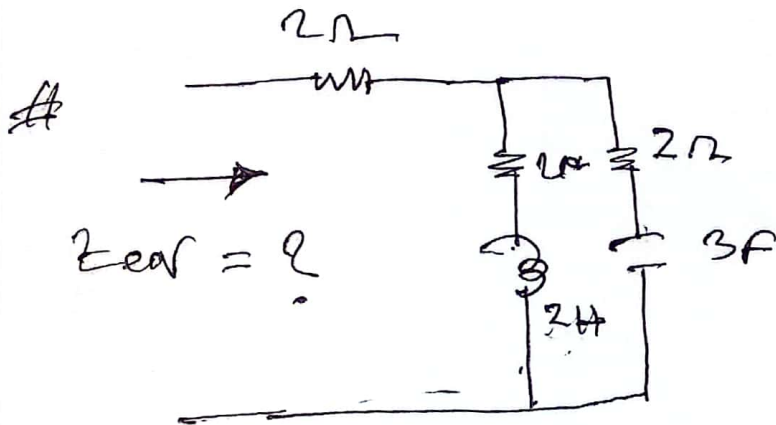

frequency = 50 Hz

$$C = 3$$

$$X_C = \frac{-j}{2\pi f_c} = \frac{-j}{2\pi \times 50 \times 3}$$

$$= -j1.06 \times 10^{-3}$$

$$\frac{2\Omega}{2+2} = 1\Omega$$

$$L = 2H$$

$$X_L = j2\pi fL = j \times 2\pi \times 50 \times 2$$

$$= j628.32$$

$$X = X_C + X_L$$

$$= -j1.06 \times 10^{-3} + j628.32$$



Impedance:

$$Z = R + X$$

$$= 1 + j628.32$$

$$= 631.019 \Omega$$

Date: _____

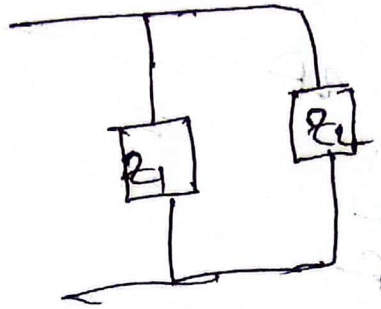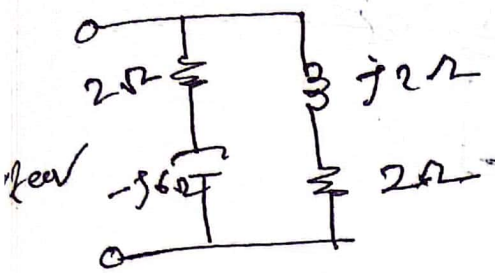


$$Z_1 = (2 - j6) \Omega$$

$$Z_2 = (2 + j2) \Omega$$


$$\begin{aligned} \therefore V_{th} &= \frac{Z_1 \times Z_2}{Z_1 + Z_2} \\ &= \frac{(2 - j6)(2 + j2)}{(2 - j6) + (2 + j2)} \\ &= 3 + j \end{aligned}$$

~~B~~

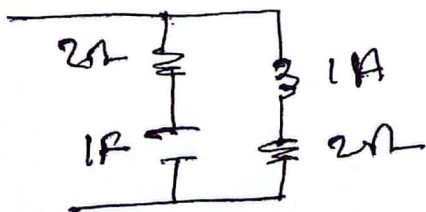

$$X_1 = \frac{1}{j\omega L} = -j \dots$$

$$X_2 = j\omega L = j \dots$$

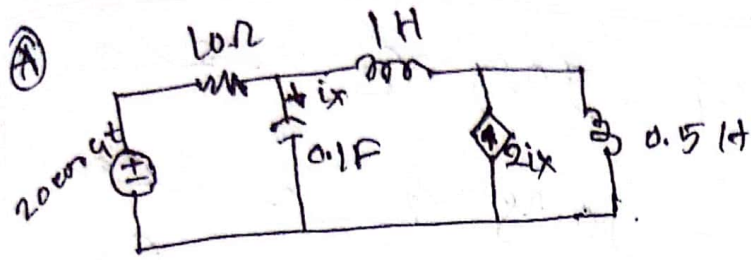

$$i_x = ?$$

$$20 \cos 4t$$

$$V_m \cos(\omega t + \phi)$$

$$V_m \angle \phi$$

$$\omega = 4$$

for $0.1 F$, $X_C = \frac{1}{j\omega C}$

$$= \frac{1}{j \times 4 \times 0.1}$$


$$= -j2.5 \Omega$$

for $1 H$, $X_L = j\omega L = j \times 4 \times 1$

$$= j4 \Omega$$

$0.5 H$, $X_L = j\omega L = j \times 4 \times 0.5$

$$= j2 \Omega$$

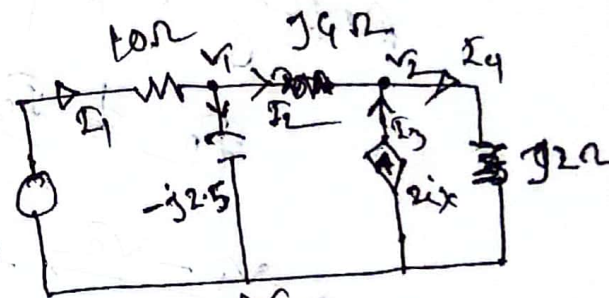

$$i_x = \frac{V_1}{-j2.5}$$

for $i_3 = i_x$

$$= \frac{V_1}{-j2.5}$$

Apply nodal analysis,

$$I_1 = I_2 + I_3$$

$$\Rightarrow \frac{20\angle 0 - V_1}{10} = \frac{V_1}{-j2.5} + \frac{V_1 - V_2}{1}$$

$$\Rightarrow 2\angle 0.1 V_1 = j0.4 V_1 - j0.25 V_1 + j0.25 V_2$$

(Div. by 10)

$$\Rightarrow -0.1 v_1 - j0.15 v_1 - j0.25 v_2 = 2 \angle 0^\circ$$

$$\Rightarrow (0.1 - j0.15) v_1 - j0.25 v_2 = 2 \angle 0^\circ \quad \text{--- (i)}$$

Apply nodal analysis in node (2)

$$I_2 + I_3 = I_4$$

$$\Rightarrow \frac{v_1 - v_2}{39} + \cancel{2ix} = \frac{v_2}{j2}$$

$$\Rightarrow \frac{v_1 - v_2}{39} + \frac{2v_1}{-j2.5} = \frac{v_2}{j2}$$

$$\Rightarrow 11 v_1 + 15 v_2 = 0 \quad \text{--- (ii)}$$

for v_1 and v_2

$$\Delta P \begin{bmatrix} -0.1 & -j0.15 & j0.25 \\ 11 & 15 & 0 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} 2 \angle 0^\circ \\ 0 \end{bmatrix}$$

$$\Delta = \begin{bmatrix} 2\angle 0 & -j0.25 \\ 0 & 15 \end{bmatrix} =$$

$$\therefore V_1 = \frac{\Delta_1}{\Delta}$$

$$V_2 = \frac{\Delta_2}{\Delta}$$

$$\left[\begin{matrix} (j\omega - \sqrt{\omega}) \sin \omega & \cos \omega \\ \sin \omega & \cos \omega \end{matrix} \right] \frac{1}{\omega} =$$

a) para $\omega = 0 \Rightarrow \sin \omega = 0$

b) para $\omega = \pi \Rightarrow \sin \omega = 0$

Date: 20-04-2024

Chapter - II :

* Ac power analysis

i) Instantaneous power: $V(t) = V_m \cos(\omega t + \theta_v) = V_m \angle \theta_v$
 $I(t) = I_m \cos(\omega t + \theta_i) = I_m \angle \theta_i$

$$P = VI$$

$$= 2 \cdot \frac{1}{2} V_m \cos(\omega t + \theta_v) I_m \cos(\omega t + \theta_i)$$

$$= \frac{V_m I_m}{2} \left[\cos(\omega t + \theta_v + \omega t + \theta_i) + \cos(\omega t + \theta_v - \omega t - \theta_i) \right]$$

$$= \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) + \frac{1}{2} V_m I_m \cos(2\omega t + \theta_v + \theta_i)$$

Avg power:

$$P = \frac{1}{T} \int_0^T P(t) dt$$

$$P = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i)$$

P.f power factor

V_m = voltage angle

I_m = current angle.

Problem: 11.1 P(999)

$$v(t) = 10 \angle 20^\circ$$

$$i(t) = 2 \angle 0^\circ$$

Here,

$$V_m = 10$$

$$I_m = 2$$

$$\theta_v = 20^\circ$$

$$\theta_i = 0^\circ$$

$$\therefore P = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i)$$

$$= \frac{1}{2} 10 \times 2 \cos(20^\circ - 0^\circ)$$

$$= \frac{1}{2} 20 \cos(0^\circ)$$

$$= 9.85 \quad \underline{\text{Ans.}}$$

N.B: $2\sqrt{2}$ $\cos 0 = 1$ \therefore $\cos 0 = 1$ \therefore $\cos 0 = 1$

Power factor:

Q.2:

$$Z = 30 - j70 \Omega$$

$$V = 120 \angle 0^\circ$$

Find $P_{avg} = ?$

Solⁿ:

$$V = 120$$

$$I = \frac{V}{Z} = \frac{120 \angle 0^\circ}{30 - j70}$$

$$= 1.57 \angle 66^\circ$$



$$\therefore I = 1.57 \angle 66^\circ$$


$$\therefore P_{avg} = \frac{1}{2} \times 120 \times 1.57 \cos(0 - 66)$$

$$= 15.7 \cos(-66)$$

$$= 6.38 \text{ Ans}$$

$$\left. \begin{array}{l} V = \text{Voltage} \\ Z = \text{Impedance} \end{array} \right\}$$

4.3

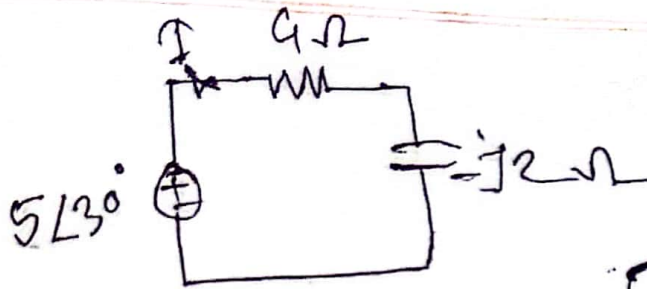

Solⁿ:

For source:

$$V = 5\angle 30^\circ$$

$$Z = 4 - j2 \Omega$$

$$I = \frac{V}{Z}$$

$$= \frac{5\angle 30^\circ}{4 - j2}$$

$$= 1.118\angle 56^\circ$$

$$P_{avg} = \frac{1}{2} V_m I_m \cos(\alpha - \theta_i)$$

$$= \frac{1}{2} * 5 * 1.118 \cos(30^\circ - 56^\circ)$$

$$= 4.47$$

$$= 2.50 \text{ W}$$

For 4Ω load:

$$I = 1.118\angle 56.56^\circ$$

$$V_R = IR$$

$$= 4 \times 1.118\angle 56.56^\circ$$

$$P_{avg} = \frac{1}{2} * 4.47 * 1.118 \cos(0)$$

$$= 2.50 \text{ W}$$

For -j2 load:

$$Z = -j2$$


$$I = 1.118\angle 56.56^\circ$$

$$V_L = (-j2) * 1.118\angle 56.56^\circ$$


$$= 2.22\angle -33.9^\circ$$

$$P_{avg} = \frac{1}{2} * 2.22 * 1.118 \cos(-33.9 - 56.56^\circ)$$

$$= 0.0066$$

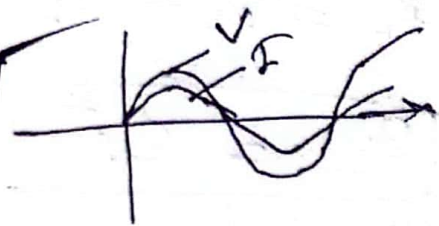

inductive load
[current lags]

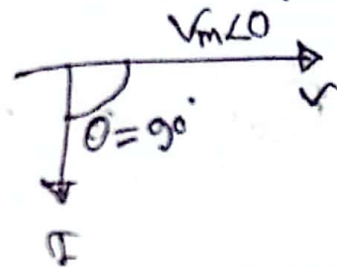

Capacitive load.
[current leads]

Ans: inductive & capacitive load
at 90° angle $P_{avg} = 0$

Date: 22-04-2


$$Z_{th} = R_{th} + jX_{th}$$

$$Z_L = R_L + jX_L$$


$$\boxed{Z_L = Z_{th}^*} = R_{th} - jX_{th}$$

$$R_L = |Z_{th}| = \sqrt{R_{th}^2 + X_{th}^2}$$

$$P_{max} = \frac{|V_{th}|^2}{8 R_{th}}$$

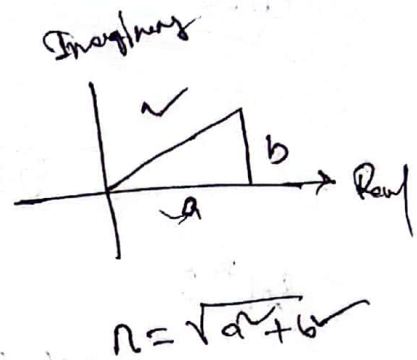

Example - 1.5 :

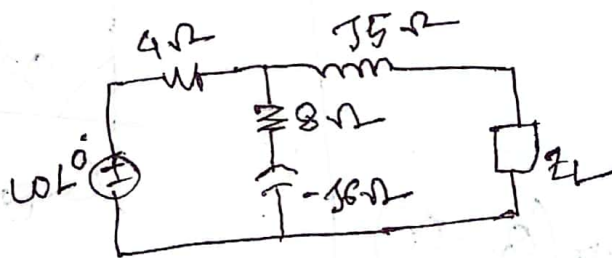


Find $Z_L = ?$

Power

Soln: For Z_{th}


$$Z_{th} = \frac{(8 - j6) \times 4}{8 - j6 + 4} + j5$$

$$= 2.93 + j9.97 \Omega$$

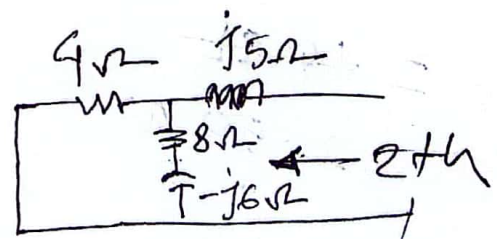

$$\therefore Z_L = Z_{th}^* = (2.93 - j4.97) \Omega$$

For V_{th} :

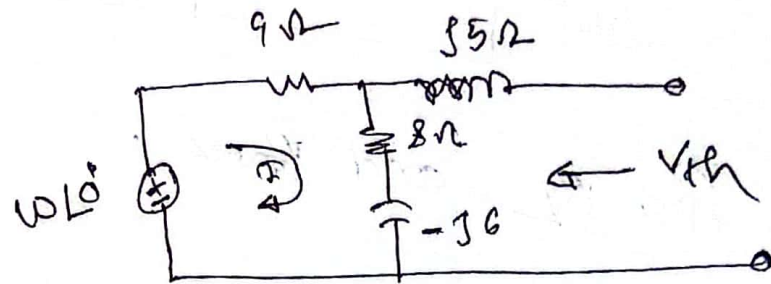

$$10\angle 0^\circ + 9I + 8I - j6I = 0$$

$$\Rightarrow 10\angle 0^\circ + 12I - j6I = 0$$

$$I = \frac{10\angle 0^\circ}{12 - j6}$$

$$V_{th} = \frac{10\angle 0^\circ}{12 - j6} \times (8 - j6)$$

$$= (7.33 - j1.33)$$

$$Z_{th} = 2\Omega$$

$$\text{Here, } Z = 8 - j6$$

$$|V_{th}| = \sqrt{(7.33)^2 + (-1.33)^2}$$

$$= 7.45 \text{ V}$$

$$\therefore P_{max} = \frac{(7.45)^2}{8 \times 2.93}$$

$$= 2.368 \text{ W}$$


Ans

11.5

$$\left| \begin{array}{l} V_{th} = 7.45 \\ R_{th} = 2.93 \end{array} \right.$$

V.V.D


P.P: 11.6

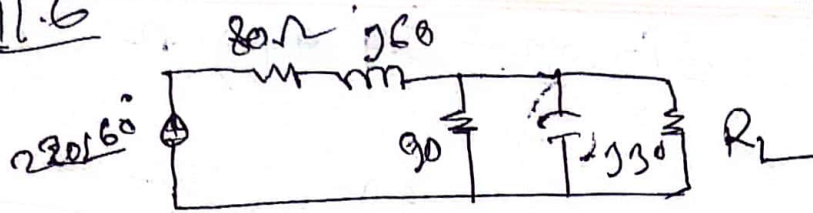

Find R_L and P_{max} .

Soln:

for Z_{th} :

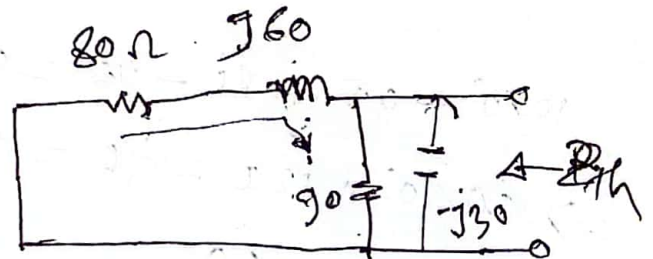

$$\begin{aligned} & \left(\frac{(80 + j60) * 90}{90 + j60} \right) + 10 \angle 30^\circ \\ \Rightarrow & 107.69 + j41.53 \\ & \downarrow \\ & R_{th} \end{aligned} \quad \begin{aligned} & \left(\frac{(80 + j60) * 90}{90 + j60} \right) + 10 \angle 30^\circ \\ & \downarrow \\ & Z_{th} \end{aligned} =$$

$$Z_{th} = 90 \parallel (-j30) \parallel (80 + j60)$$

$$= \frac{90 * -j30}{90 + (-j30)}$$

$$= (9 - j27) \Omega \parallel (80 + j60)$$


$$= \frac{(9 - j27) * (80 + j60)}{(9 - j27) + (80 + j60)}$$

$$= \cancel{8091 - 1620j - 2160j + 1620} \\ = 17.90 - j2.99$$

~~Now~~

$$\text{Now } R_L = |Z_{th}| = \sqrt{(17.90)^2 + (-2.99)^2} \\ = 30 \Omega$$


For V_{th} :

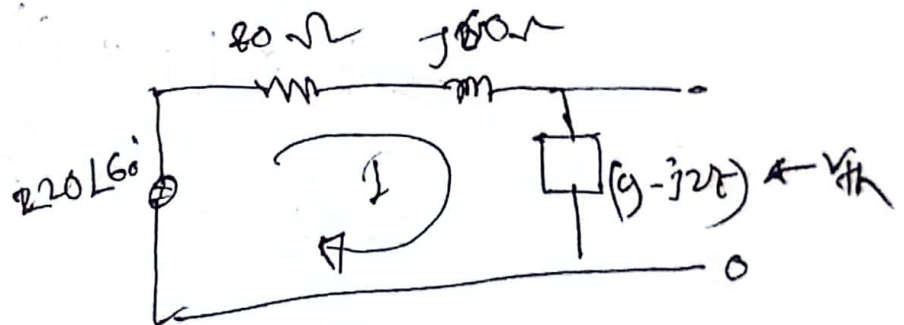

$$-220\angle 60^\circ + (80 + j60)I + (9 - j27)I = 0$$

$$I = \frac{220\angle 60^\circ}{80 + j60 + 9 - j27}$$

$$= 1.78 + j1.47$$

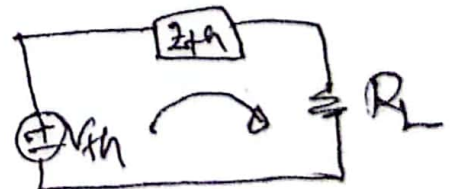

$$V_{th} = (1.78 + j1.47)(9 - j27) = 55.71 - j34.83 \\ = 65.7\angle -32.01^\circ$$

$$I = \frac{V_{th}}{Z_{th} + R_L}$$

$$= \frac{65.7 \angle -32.01^\circ}{(17.90 - j29.9) + 30}$$

$$\frac{6+j}{6+j} + 5$$

$$= 8.23 \Omega$$

$$= 1.24 - j0.095$$

$$-16 + 4i + 6i = 0$$

$$|I| = 1.24$$

$$= \omega L = 46$$

$$P_{max} = \frac{1}{2} |I|^2 R_L$$


$$\therefore I = \frac{46}{\omega}$$

$$= \frac{1}{2} \times (1.24)^2 \times 30$$

$$= 1.6$$

$$= 23.06 \text{ W (Am)}$$

$$V =$$

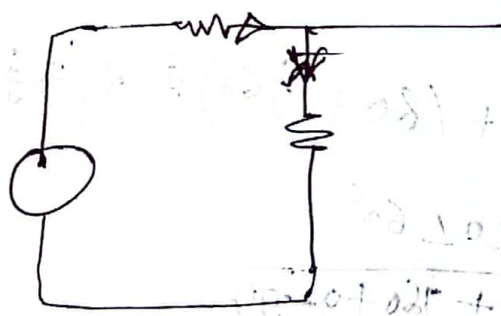

$$28.98 - 15.00 = (10 - 0) (10 - 0) + 0.1 = 13.98$$