

Northern University Bangladesh



Lab report: 02

Department: CSE

Course title: Digital Electronics & Pulse Technique Lab Work

Experiment no: CSE 2366

Experiment name: Implement Diode Register Logic AND, OR and NOT gate in Tinkercad

Submitted by

Submitted to

Name: Fardeen Ahmed

Id: 41210301615

Date of Experiment: 10/6/2024

Date of submission: 22/6/2024


Name of teacher: Nizia Nahyan

Designation: Lecturer


Signature:

DRL AND gate

Circuit diagram:

 

Circuits Screenshot:

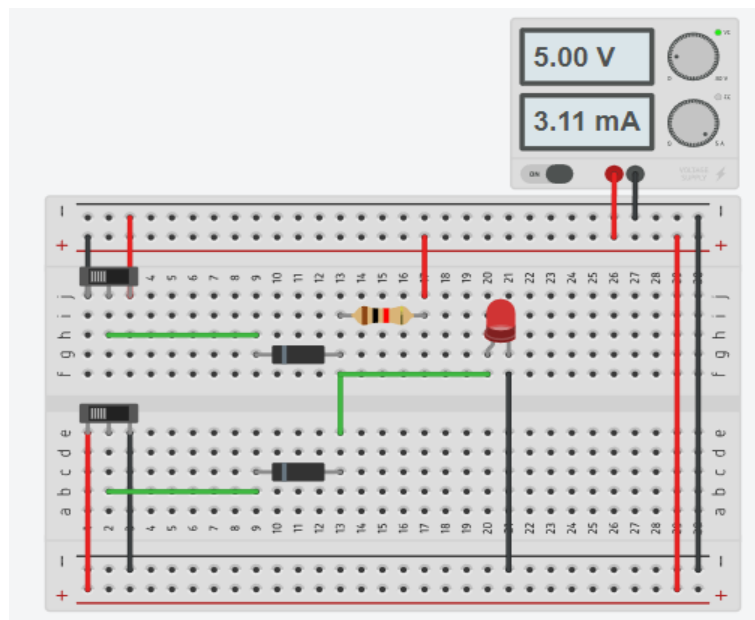


Tinkercad circuit link:


https://www.tinkercad.com/things/0M60e5Ftp00-drl-and-gate-1615?sharecode=U_oHK8NgMZTldVPNzLoqu8tAqYxAOJa_li8h34nqDsg

DRL OR gate

Circuit diagram:

 

Circuit screenshot:

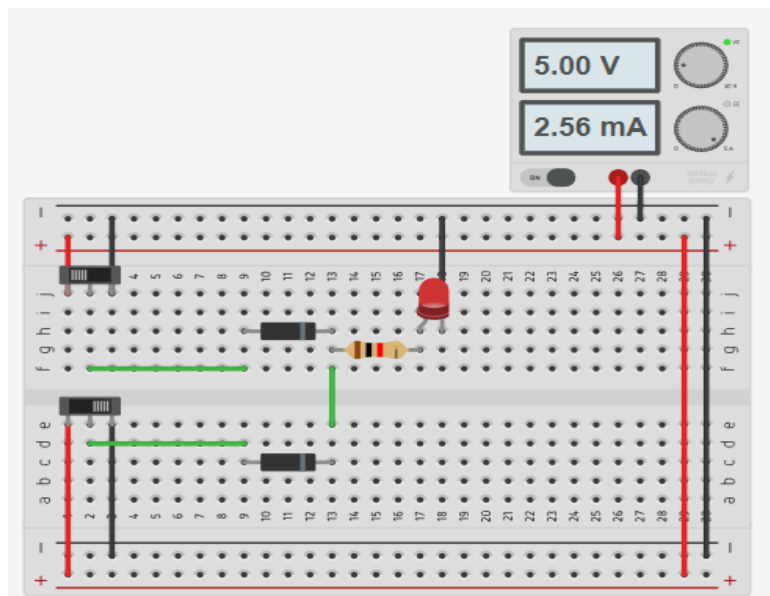


Tinkercad circuit link:


https://www.tinkercad.com/things/37vQ5VAtfZG-drl-or-gate-1615?sharecode=SsDHrRljnQ_2Fh0d1eu62u5WvcSm0xFriwkUzojUw_M

DRL NOT gate

Circuit diagram:

 

Circuit screenshot:

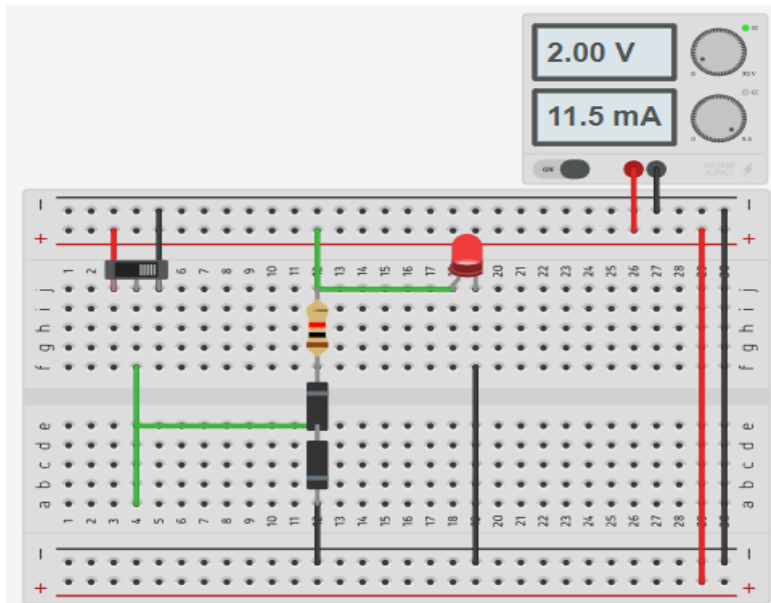

Tinkercad circuit link:

<https://www.tinkercad.com/things/dTpGLXZBjav-drl-not-gate-1615?sharecode=jBjhTpjTsVocOSnPafBePKY6huXse9GyyWZn5rx9Fnw>