




# **CMOS VLSI Design**

## Digital Design

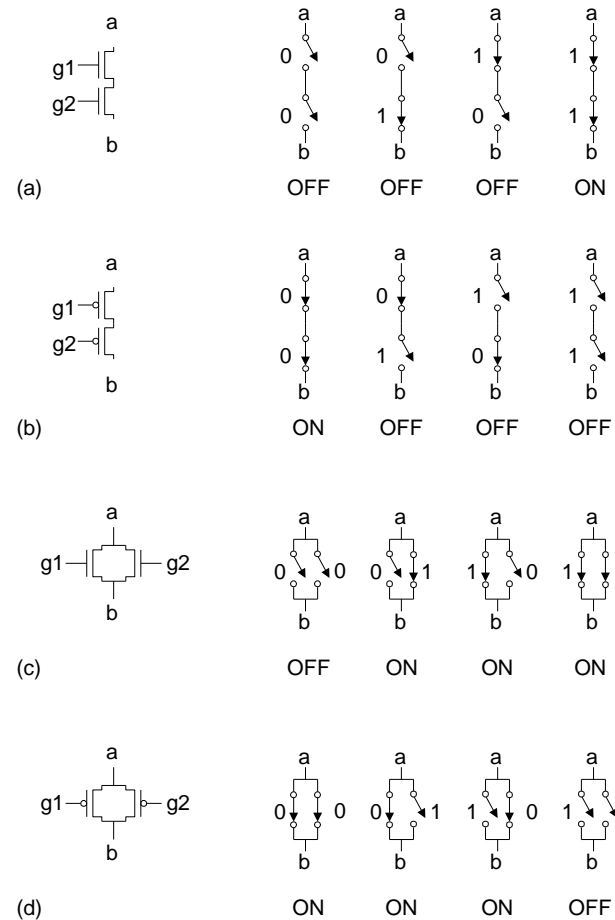
# Series and Parallel

- ❑ nMOS: 1 = ON
- ❑ pMOS: 0 = ON
- ❑ *Series*: both must be ON
- ❑ *Parallel*: either can be ON





 
# Conduction Complement

- ❑ Complementary CMOS gates always produce 0 or 1
- ❑ Ex: NAND gate
  - Series nMOS:  $Y=0$  when both inputs are 1
  - Thus  $Y=1$  when either input is 0
  - Requires parallel pMOS
- ❑ Rule of *Conduction Complements*
  - Pull-up network is complement of pull-down
  - Parallel  $\rightarrow$  series, series  $\rightarrow$  parallel



   
# Compound Gates

- ❑ *Compound gates can do any inverting function*
- ❑ Ex:  $Y = (A.B + C.D)'$




# Example:


$$\square Y = ((A+B+C).D)'$$

# Example:

$$\square Y = ((A+B+C).D)'$$

 


# CMOS Gate Design

- Activity:
  - Sketch a 3-input CMOS NAND gate

 
## 3-input NAND Gate

- Y pulls low if ALL inputs are 1
- Y pulls high if ANY input is 0



 
# CMOS Gate Design

- Activity:
  - Sketch a 4-input CMOS NOR gate





# Example: $A+(BC)$

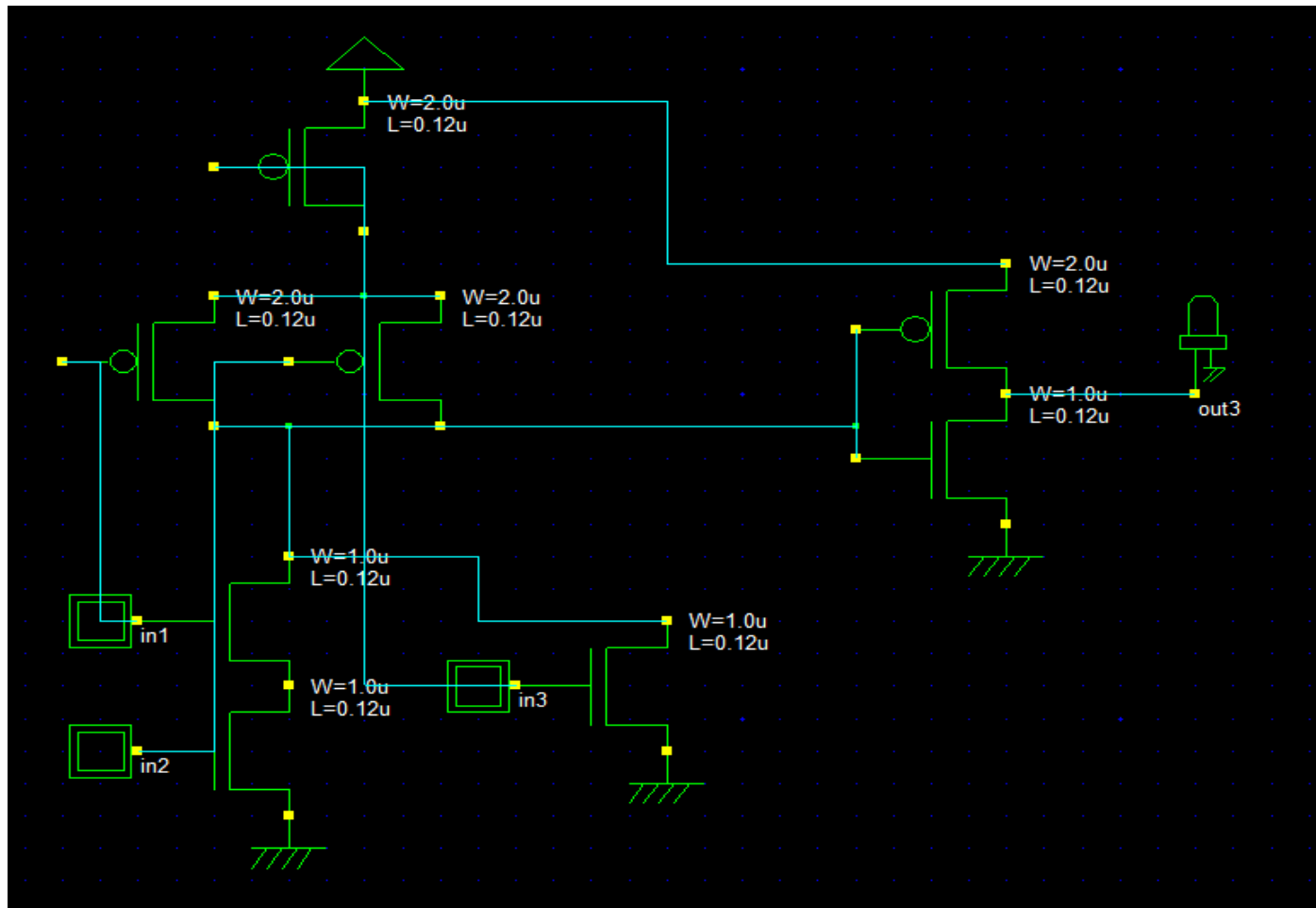




## ► Realization of More Complicated Gate Circuits

### ► a) $Y = \overline{A(B+C)}$

- Transistor Level



- It need only 6 transistors

 

## Constructing Complex Gates

  Example:  $F = \overline{(A \cdot B) + (C \cdot D)}$

- ④ Construct P-network by taking complement of N-expression  $(AB + CD)$ , which gives the expression,  $(\overline{A} + \overline{B}) \cdot (\overline{C} + \overline{D})$
- ⑤ Combine P and N circuits



## Example of Compound Gate

$$F = \overline{(A + B + C) \cdot D}$$


Note:

N- and P- graphs are duals of each other


In this case, the function is the complement of the switching function between F and GND

Question: Does it make any difference to the function if the transistor with input D is connected between the parallel A, B, C, transistors and GND?

What about the electrical behavior?

 


## Example of More Complex Gate

 

$$OUT = \overline{(A + B) \cdot (C + D) \cdot (E + F + (G \cdot H))}$$


## Example of More Complex Gate

 

$$OUT = \overline{(A + B) \cdot (C + D) \cdot (E + F + (G \cdot H))}$$
 
# Complementary CMOS

- ❑ Complementary CMOS logic gates
  - nMOS *pull-down network*
  - pMOS *pull-up network*
  - a.k.a. static CMOS




# CMOS Device Structure

⌘ For every CMOS device, there are essentially two separate circuits:

- 1) *The Pull-Up Network*
- 2) *The Pull-Down Network*

The basic CMOS structure is:

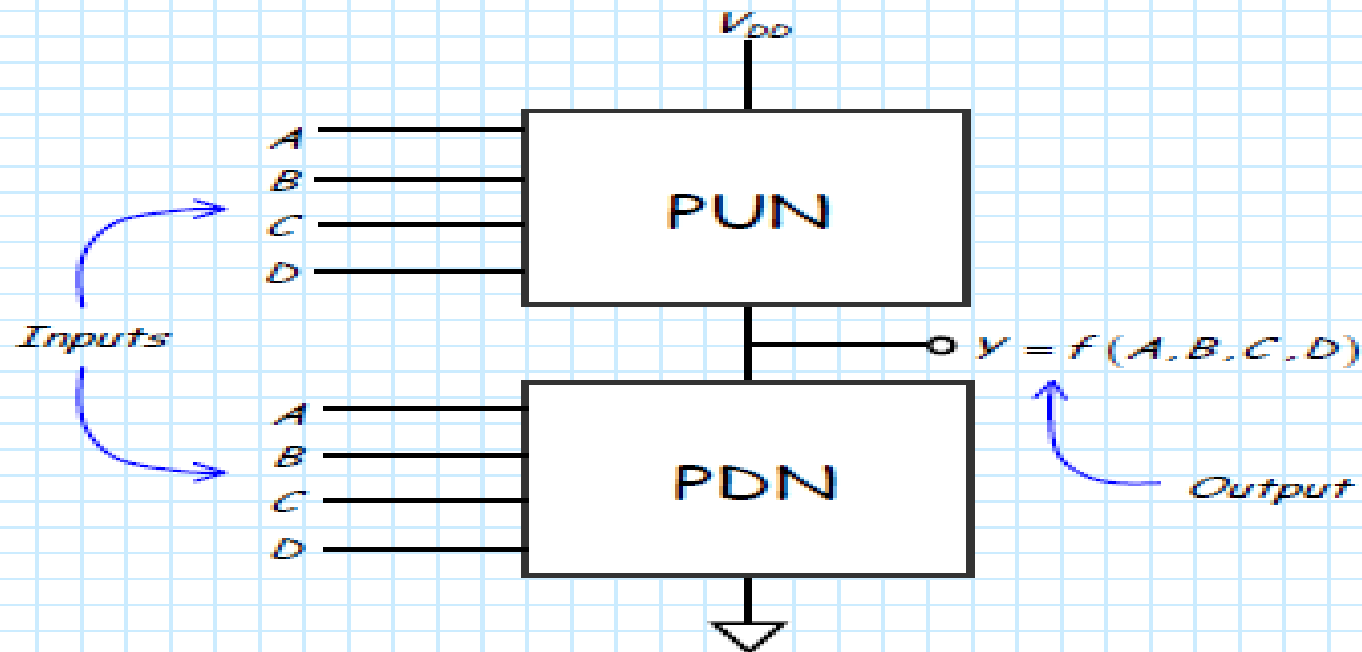


⌘ A CMOS logic gate must be in one of two states!




 
# Stick Diagrams

- ❑ *Stick diagrams* help plan layout quickly
  - Need not be to scale
  - Draw with color pencils or dry-erase markers





 
 
# Pseudo-nMOS

- ❑ In the old days, nMOS processes had no pMOS
  - Instead, use pull-up transistor that is always ON
- ❑ In CMOS, use a pMOS that is always ON
  - *Ratio* issue
  - Make pMOS about  $\frac{1}{4}$  effective strength of pulldown network


    
# Dynamic Logic

- ❑ *Dynamic* gates uses a clocked pMOS pullup
- ❑ Two modes: *precharge* and *evaluate*




# Sequencing

## ❑ *Combinational logic*


- output depends on current inputs
 
## ❑ *Sequential logic*

- output depends on current and previous inputs
- Requires separating previous, current, future
- Called *state* or *tokens*
- Ex: FSM, pipeline



Finite State Machine

 

Pipeline

# ROM Example

## ❑ 4-word x 6-bit ROM



- Represented with dot diagram
- Dots indicate 1's in ROM

Word 0: 010101

Word 1: 011001

Word 2: 100101

Word 3: 101010

  

Looks like 6 4-input pseudo-nMOS NORs


# PLAs

- ❑ A *Programmable Logic Array* performs any function in sum-of-products form.
- ❑ *Literals*: inputs & complements
- ❑ *Products / Minterms*: AND of literals
- ❑ *Outputs*: OR of Minterms

- ❑ Example: Full Adder

$$s = a\bar{b}\bar{c} + \bar{a}b\bar{c} + \bar{a}\bar{b}c + abc$$

$$c_{\text{out}} = ab + bc + ac$$

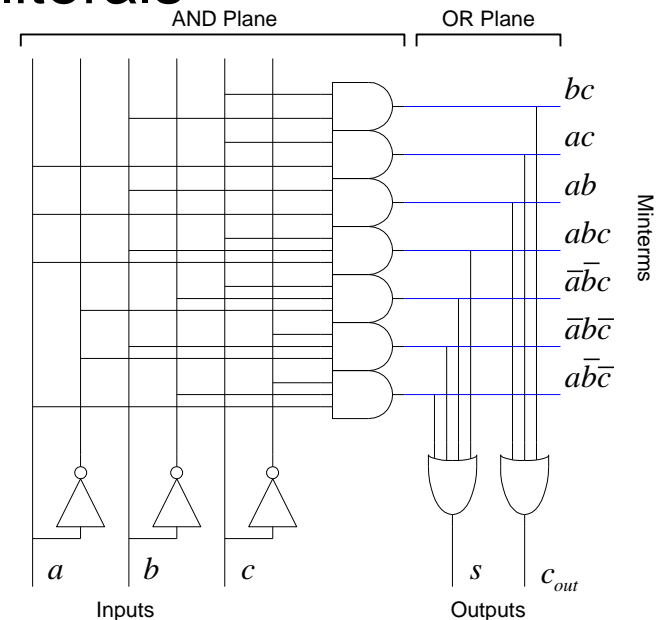

# PLA Schematic & Layout

